


CS211: Computer Organisation
Semester 1, 2025

Assignment #3 (Weight: 5%)

Due: 4:00pm Fiji Time, Friday 30th May, 2025

Learning Outcome: Build a simple digital circuit.

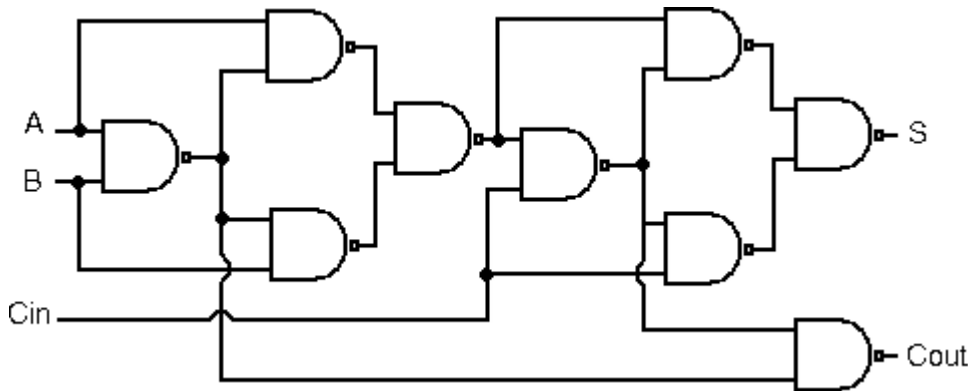Implement the following circuit using LogiSim and construct the truth table for it.



Submission Guidelines

- **This assignment is to be completed individually.**
- Submit two files by zipping which has the logisim file and word document for the truth table.
- Only **one** submission is required – rename the file as your id number.
- A **softcopy** of your assignment should be submitted through **Moodle Drop Box**.
- Incorrect/incomplete submissions or any assignments caught as plagiarized work will receive a mark of zero (0).
- Late submissions will **not** be accepted unless prior arrangements have been made with the lecturer and supplemented by documentary evidence.
- Do not submit any piece of assignment work on Moodle Discussion Forums.

The following rubric will be used to mark your assignment. This rubric assumes **no late submission**.

	CBOK	Unsatisfactory	Satisfactory	Good	Total Score
Circuit Construction and Truth Table	Abstraction	Partially constructed circuit. [1 mark]	Partially constructed circuit with truth table. [3 marks]	Properly implemented circuit with truth table. [5 marks]	